

# Gate Assignment

SAMMETA SAIPOORNA  
EE23BTECH11055

## Question

The voltage source  $V_s = 10\sqrt{2}\sin(20000\pi t)$  V has an internal resistance of 50 ohms. The RMS value of the current through  $R$  is \_\_\_\_ (in mA) (rounded off to one decimal place).

## Solution

$$V_s = 10\sqrt{2}\sin(20000\pi t) \text{ volts} \quad (1)$$

$$R_{\text{internal}} = 50 \text{ ohms} \quad (2)$$

$$R = 25 \text{ ohms} \quad (3)$$

$$Z = R + R_{\text{internal}} = 25 + 50 = 75 \Omega \quad (4)$$

$$I_{\text{RMS}} = \frac{V_{\text{RMS}}}{Z} \quad (5)$$

$$V_{\text{RMS}} = \frac{10\sqrt{2}}{\sqrt{2}} = 10 \text{ volts} \quad (6)$$

$$I_{\text{RMS}} = \frac{10}{75} \times 1000 = \frac{2000}{15} \approx 133.3 \text{ mA} \quad (7)$$